

AC-Coupling Between Differential LVPECL, LVDS, HSTL, and CML

Kal Mustafa/Chris Sterzik

High Performance Analog

ABSTRACT

This report provides a quick reference of ac-coupling techniques for interfacing between different logic levels. The four differential signaling levels found in this report are low-voltage positive-referenced emitter coupled logic (LVPECL), low-voltage differential signals (LVDS), high-speed transceiver logic (HSTL), and current-mode logic (CML). From these four differential signaling levels, 16 interface cases are provided.

Contents

1	AC-Coupling	2
2	References	16

List of Figures

1	AC-Coupling to Shift Common-Mode Voltage	2
2	Input and Output Parameters	2
3	LVPECL to LVPECL.....	3
4	LVPECL to LVPECL.....	4
5	LVPECL to LVDS	4
6	LVPECL to CML	5
7	LVPECL to CML Converter.....	5
8	LVPECL to HSTL	6
9	LVDS to LVPECL	6
10	LVDS to LVPECL	7
11	LVDS to LVDS	7
12	LVDS to LVDS	8
13	LVDS to CML	8
14	LVDS to CML Translator.....	9
15	LVDS to HSTL	9
16	CML to LVPECL	10
17	CML to LVPECL	10
18	CML to LVDS	11
19	CML to LVDS	11
20	CML to CML	12
21	CML to HSTL	12
22	CML to HSTL	13
23	HSTL to LVPECL	13
24	HSTL to LVPECL Converter	13
25	HSTL to LVDS	14
26	HSTL to LVDS	14
27	HSTL to LVDS Converter	14
28	HSTL to CML	15
29	HSTL to HSTL	15
30	HSTL to LVPECL to HSTL Using the CDCLVP110	16

List of Tables

1	Typical LVPECL, LVDS, HSTL, and CML Outputs	3
2	Typical LVPECL, LVDS, CML, and HSTL Input Levels	3
3	Interface Table	3

1 AC-Coupling

AC-coupling is used to change the common-mode voltage level when interconnecting different physical layers. A simple example is shown in [Figure 1](#).

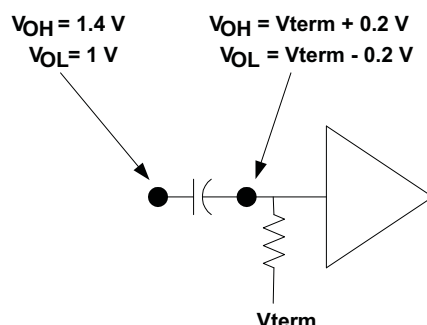


Figure 1. AC-Coupling to Shift Common-Mode Voltage

The capacitor in [Figure 1](#) removes the dc component of the signal (common-mode voltage), while the ac component (voltage swing) is passed on. The resistor to V_{term} in [Figure 1](#) represents the biasing structure used to set the common-mode voltage on the receiver side of the ac-coupling capacitor. Throughout this document the capacitor value is 10nF and the biasing structure is either part of the internal biasing of the receiver or an external resistor pull-up and/or pull-down network.

In high-speed applications, ac-coupling is only recommended for dc-balanced signals. AC coupling generates base-line wander in high-speed serial data transmission which is non-dc balanced. Examples of dc-balanced signals are 50% duty cycle clocks, Manchester-coded data, and ANSI fiber channel 8B/10B encoded data.

The more common physical layers (PHYs) that appear in the telecom industry are LVDS, LVPECL, HSTL, and CML. In order to interface these different PHYs, it is important to understand the input and output levels of each. The output and input levels for each of the PHYs are found in [Table 1](#) and [Table 2](#) respectively, and the output and input levels are illustrated in [Figure 2](#).

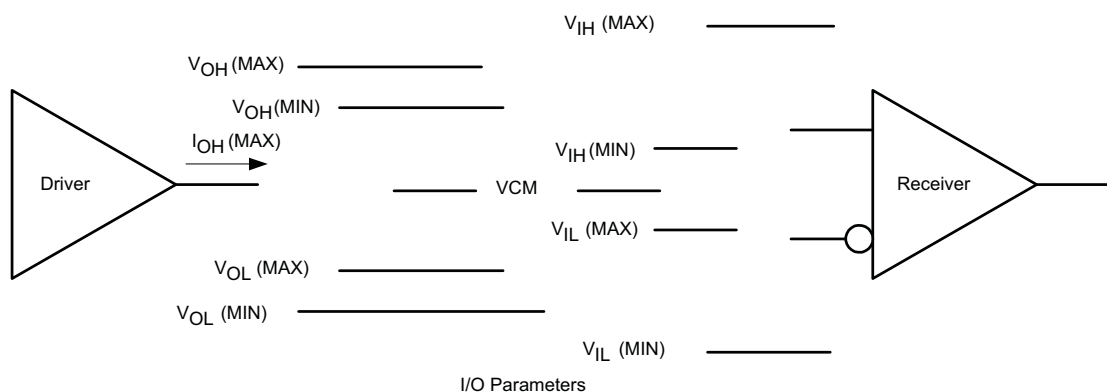


Figure 2. Input and Output Parameters

Table 1. Typical LVPECL, LVDS, HSTL, and CML Outputs

OUTPUT	LVPECL	LVDS	HSTL	CML
V_{OH} (Min)	2.275 V	1.249	$V_{DDQ}^{(1)} - 0.4$	$V_{CC}^{(2)}$
V_{OL} (Max)	1.68 V	1.252	0.4	$V_{CC} - 0.4$ V

(1) $V_{DDQ} = 1.5$ V $\pm 10\%$.

(2) $V_{CC} = 3.3$ V $\pm 10\%$

Table 2. Typical LVPECL, LVDS, CML, and HSTL Input Levels

INPUT	LVPECL	LVDS	HSTL	CML
V_{IH} (Min)	2.135 V	1.249	$V_{Ref} + 0.2$	V_{CC}
V_{Ref} or V_{CM}	2	1.2	0.75	$V_{CC} - 0.2$ V
V_{IL} (Max)	1.825 V	1.252	$V_{Ref} - 0.2$	$V_{CC} - 0.4$ V
V_{ID} (Min)	310 mV	200 mV	400 mV	400 mV

The only standardized PHY is LVDS (TIA/EIA-644A); therefore, the interface circuits in this document are only recommended for devices that coincide with the values in Table 1 and Table 2. The devices listed as examples in each interface circuit have been verified in bench testing with 10nF ac-coupling capacitors.

Table 3. Interface Table

FROM		TO		
	LVPECL	LVDS	CML	HSTL
LVPECL	See Figure 3 or Figure 4	See Figure 5	See Figure 6 or Figure 7	See Figure 8
LVDS	See Figure 9 or Figure 10	See Figure 11 or Figure 12	See Figure 13 or Figure 14	See Figure 15
CML	See Figure 16 or Figure 17	See Figure 18 or Figure 19	See Figure 20	See Figure 21 or Figure 22
HSTL	See Figure 23 or Figure 24	See Figure 25, Figure 26, or Figure 27	See Figure 28	See Figure 29

1.1 LVPECL

The 150- Ω resistor is used to bias the LVPECL output (at $V_{CC} - 1.3$ V) as well as provide a dc current path for the source current. The pull-up and pull-down combination terminates the 50- Ω transmission line and establishes the LVPECL common-mode voltage of 2 V at the receiver.

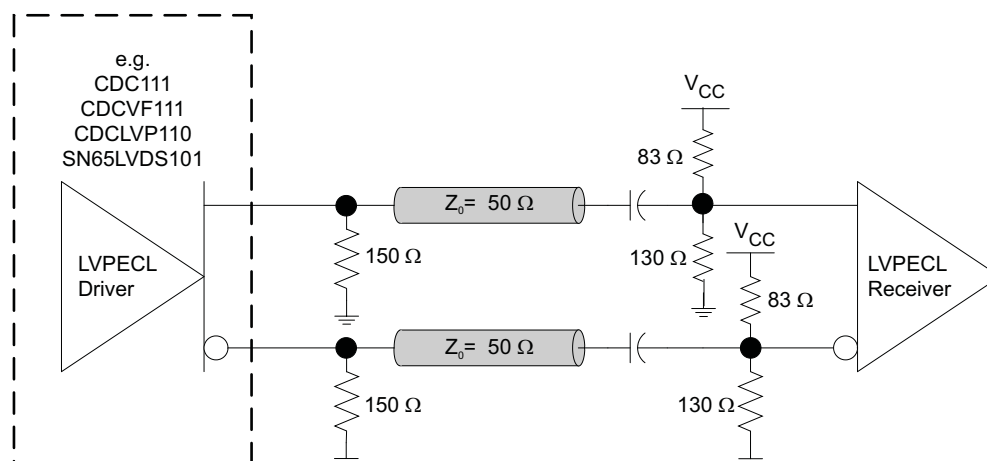


Figure 3. LVPECL to LVPECL

Once again, the 150- Ω resistors are used to bias the LVPECL output (at $V_{CC} - 1.3$ V) and provide a dc-current path for the source. The split termination with a capacitor is useful in eliminating common-mode noise manifested as differential skew between the true and complementary signals. The VBB output is provided on most LVPECL receivers.

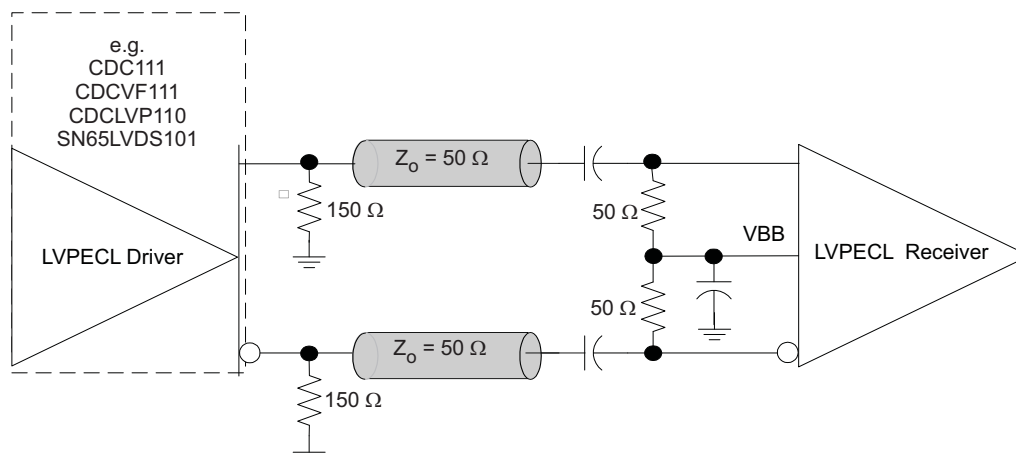


Figure 4. LVPECL to LVPECL

The 150-Ω resistor is used to dc-bias the LVPECL output (at $V_{CC} - 1.3$ V) as well as provide a dc current path for the source current. The external 100Ω is used to terminate the differential 100-Ω transmission line impedance as well as provide sufficient signal swing to drive the wide common-mode LVDS receivers. The two 10kΩ resistors set the receiver common-mode voltage to 1.65V, which is within the common-mode voltage range of an LVDS receiver (see TIA/EIA-644). For LVDS receivers with integrated 100-Ω termination the external 100-Ω resistor in Figure 5 is not required (e.g., SN65LVDT33, SN65LVDT100, and SN65LVDT122).

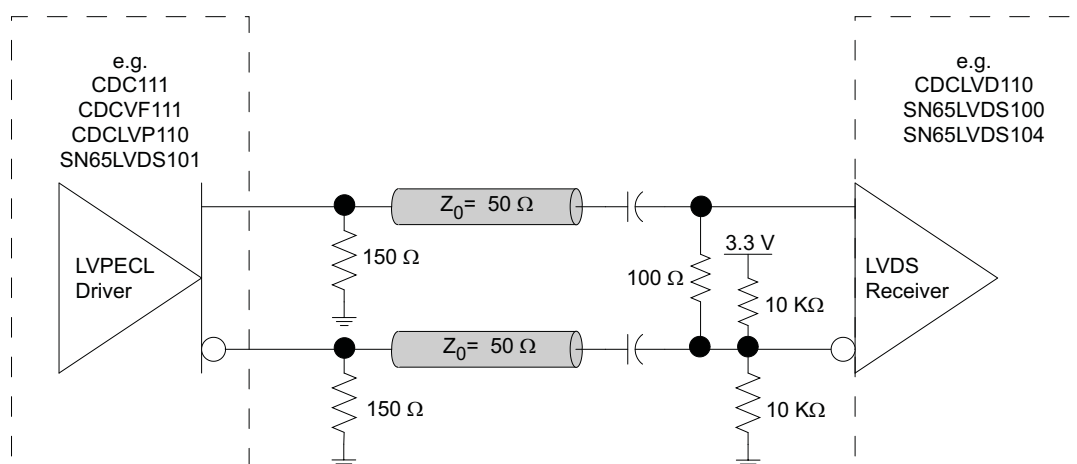


Figure 5. LVPECL to LVDS

In Figure 6, there are two resistors, the 150Ω (R-bias) and R_a . The 150-Ω resistor is required to dc-bias the LVPECL outputs prior to ac-coupling. The value of R-bias ranges from 140Ω to 240Ω. In the case where the differential LVPECL output is larger than what the CML receiver can tolerate, then R_a should be used to attenuate the LVPECL output such that it meets the input voltage required for the CML receiver.

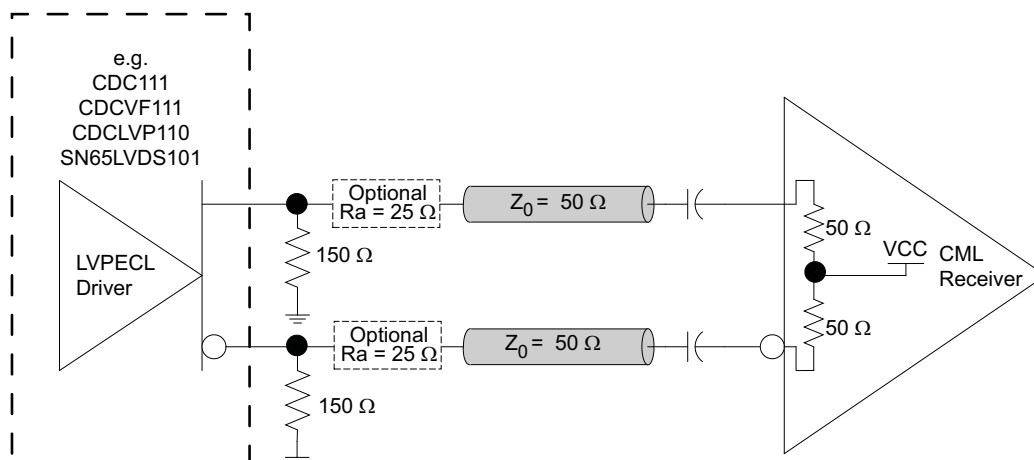


Figure 6. LVPECL to CML

For example, if the LVPECL output swing is 750 mV and the required CML receiver input is 400 mV, then the attenuation factor is 0.68, which requires $R_a \cong 23\Omega$. In Figure 6 the CML receiver is assumed to be self-biased.

The SN65CML100 in Figure 7 can be used as an LVPECL to CML converter. The 50-Ω pull-up resistors are required to bias the SN65CML100 outputs. The coupling capacitors on the inputs (optional, but shown for completeness) are used assuming that the LVPECL source is properly terminated.

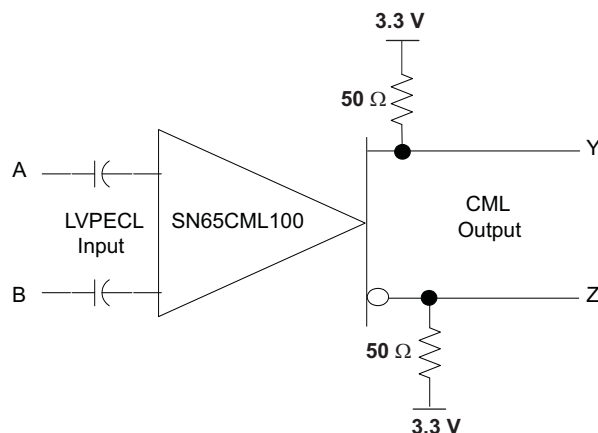


Figure 7. LVPECL to CML Converter

The 150-Ω resistor is used to bias the LVPECL output (at $V_{CC}-1.3\text{ V}$) as well as provide a dc current path for the source. The equivalent 50-Ω Thevenin resistors of R1 and R2 are used to terminate the trace impedance as well as to set the common-mode voltage ($V_{CM} = 0.75\text{ V}$) for the HSTL receiver, Figure 8.

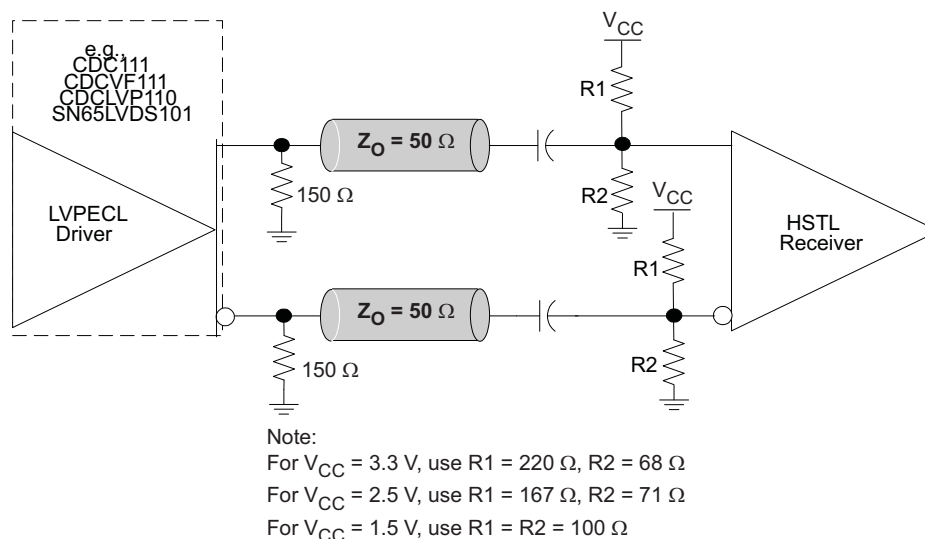


Figure 8. LVPECL to HSTL

The Thevenin equivalent of the 83 Ω and 130 Ω in [Figure 9](#), matches the 50- Ω transmission line impedance as well as sets the common-mode voltage ($V_{CM} = 2\text{ V}$) for the LVPECL receiver.

1.2 LVDS

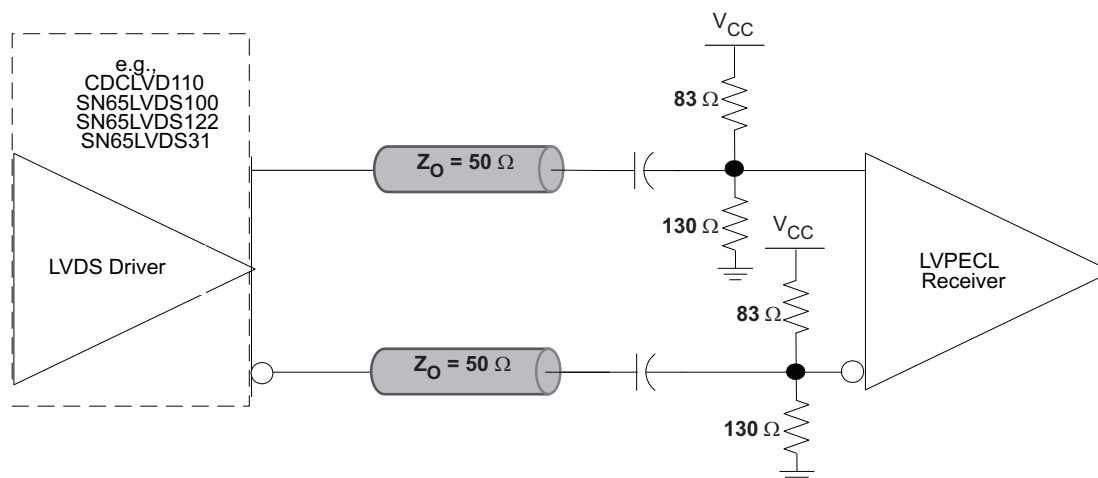


Figure 9. LVDS to LVPECL

[Figure 10](#) is recommended when V_{BB} is available on the LVPECL receiver. The split termination with the capacitor to ground is useful in eliminating common-mode noise manifested as differential skew between the true and complementary signals.

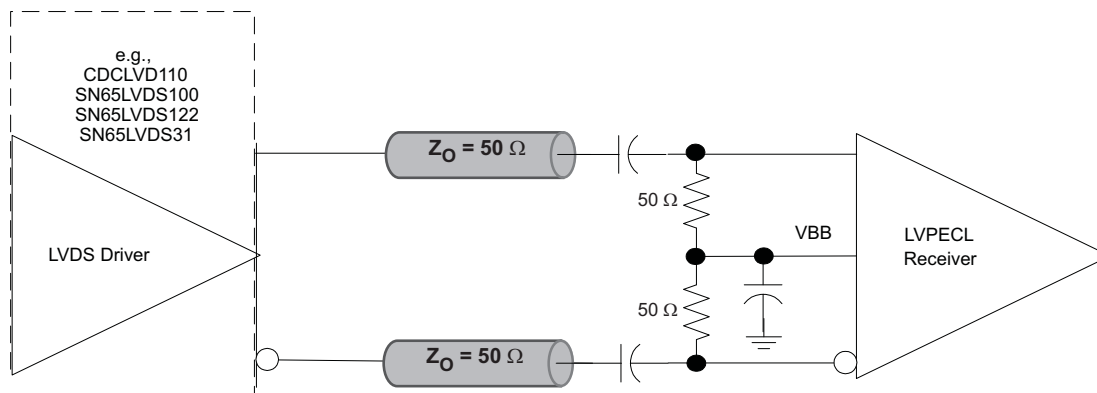


Figure 10. LVDS to LVPECL

In [Figure 11](#) is a combination of the more common 100- Ω termination and ac-coupling. It also assumes that the LVDS receiver does not include on-chip termination.

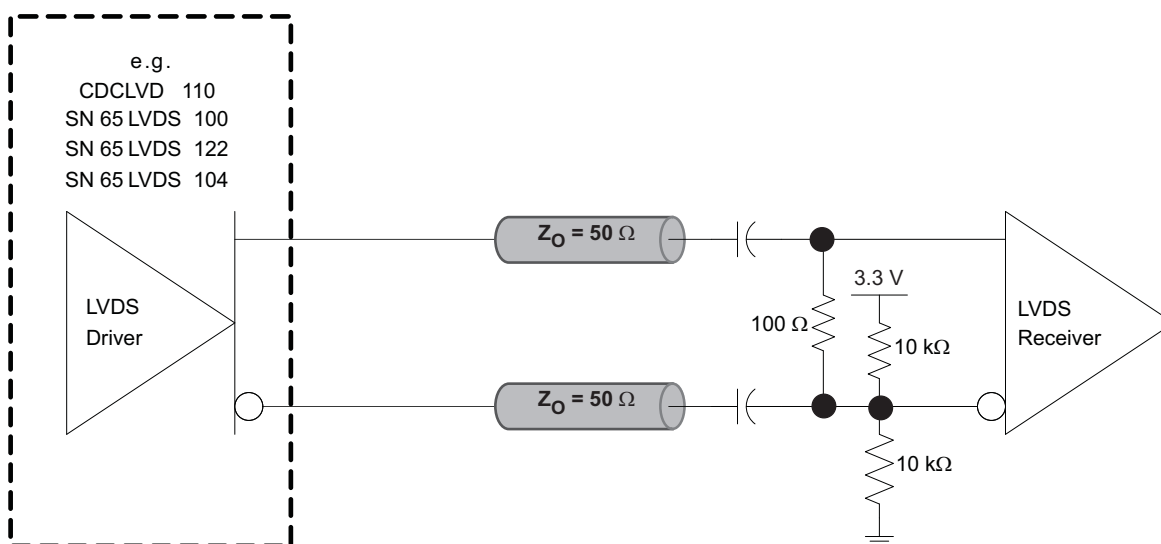


Figure 11. LVDS to LVDS

[Figure 12](#) has an advantage over [Figure 11](#) of correcting for (differential) skew mismatch between the true and complementary signals. Both [Figure 11](#) and [Figure 12](#) assume that the LVDS receiver is self-biased.

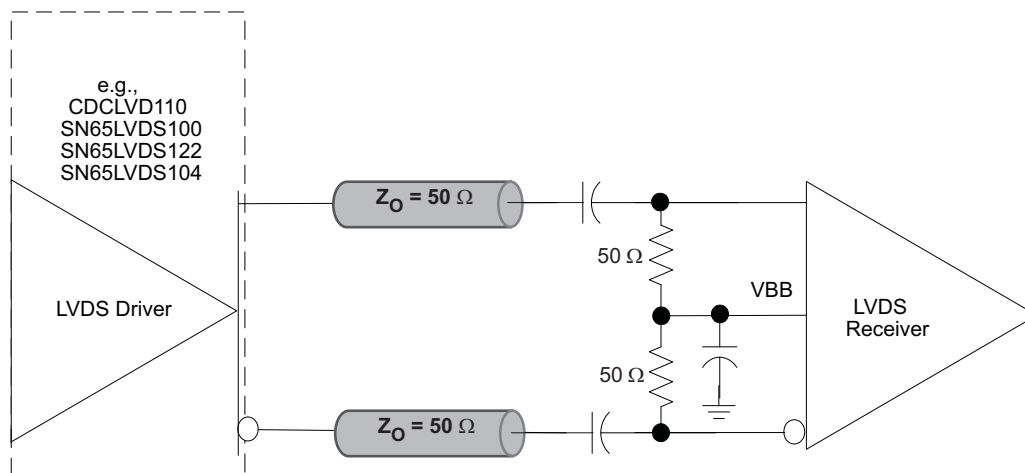


Figure 12. LVDS to LVDS

Most CML receivers have an on-chip termination, and there is no need for additional resistors to terminate the transmission line. The two 10-k Ω resistors are only required if the CML receiver is not self-biased and may vary from one vendor to another; see the manufacturer's data sheet for details.

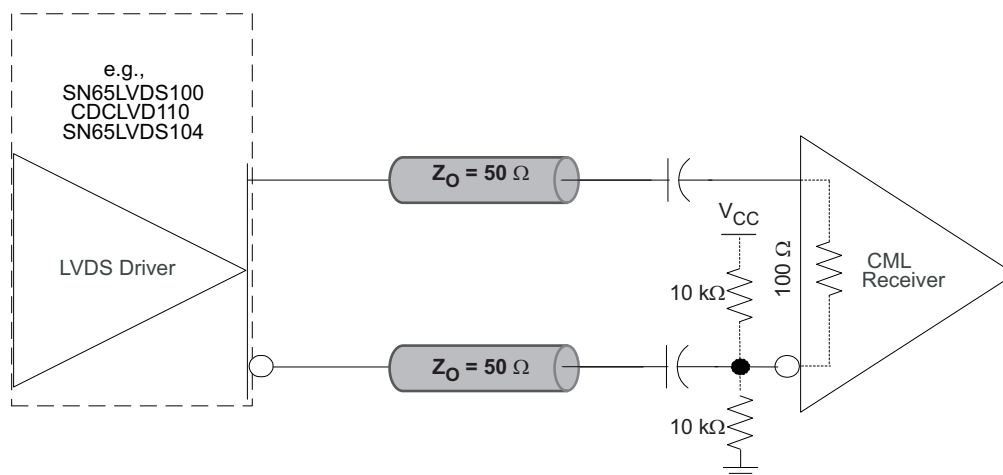


Figure 13. LVDS to CML

The SN65CML100 has a wide-common mode receiver, which allows the device to be used as an LVDS to CML translator. Two 50- Ω pull-up resistors are required to terminate the trace and bias the SN65CML100 output stage, as shown [Figure 14](#). [Figure 14](#) implies that the LVDS input is properly terminated.

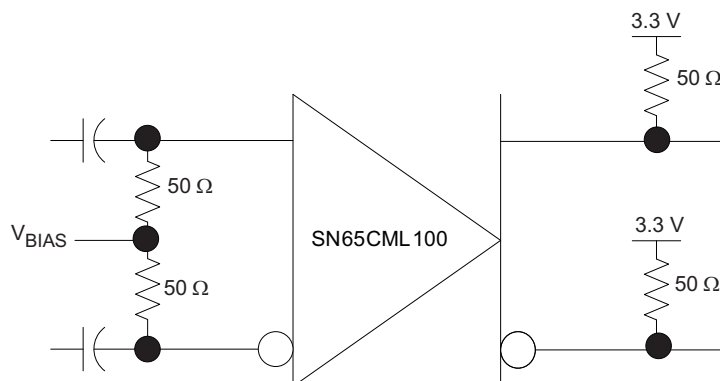


Figure 14. LVDS to CML Translator

The value of the two resistors, R1 and R2 depends on the receiver supply voltage and the common-mode voltage range of the receiver. If the HSTL receiver has a 1.5-V supply, then R1 and R2 are 100Ω each (50Ω equivalent) to terminate the trace. For other supply voltages (see the note in [Figure 15](#)) R1 and R2 should be chosen such that their parallel combination matches the transmission line and the mid-point is set to the common-mode of the HSTL receiver ($V_{CM} = 0.75\text{ V}$).

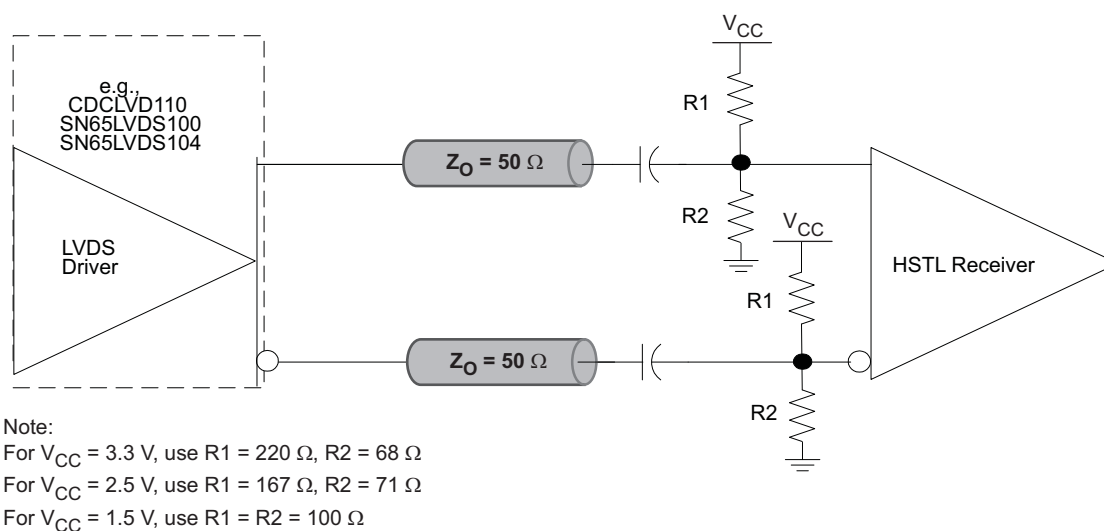


Figure 15. LVDS to HSTL

1.3 CML

The 50-Ω pull-up resistors are used to dc-bias the CML outputs and provide a source termination to match the transmission line. Figure 16 assumes that the LVPECL input stage is self-biased.

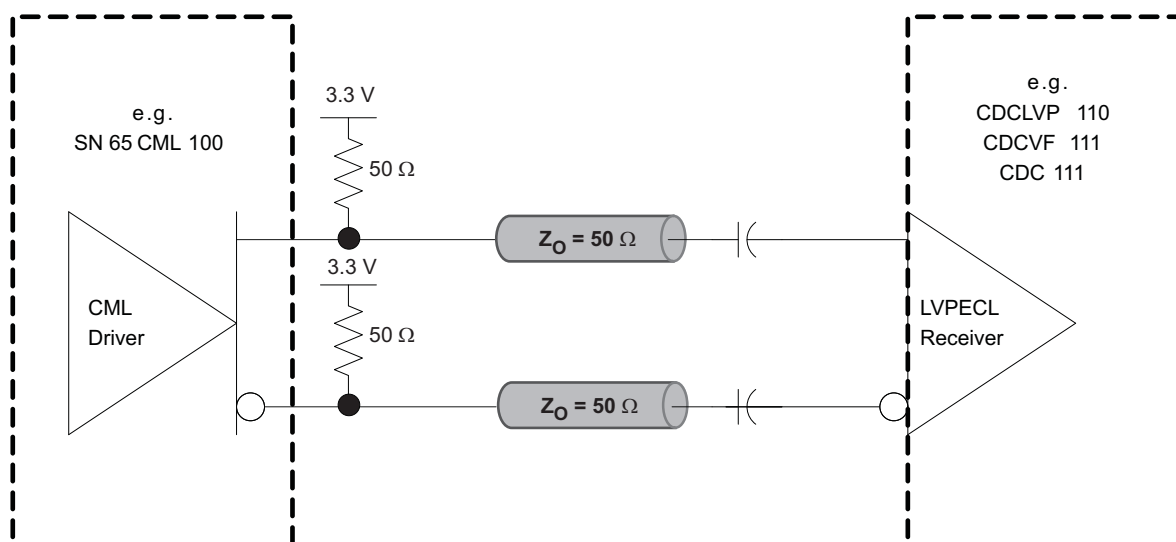


Figure 16. CML to LVPECL

The 50-Ω pull-up resistors are required for the SN65CML100 to bias and source-terminate the transmission line. R1 in Figure 17 should be larger than 50Ω in case the CML output stage losses, in addition to the PCB losses, are too high to meet the minimum differential input voltage (VID) swing requirement of the LVPECL input stage.

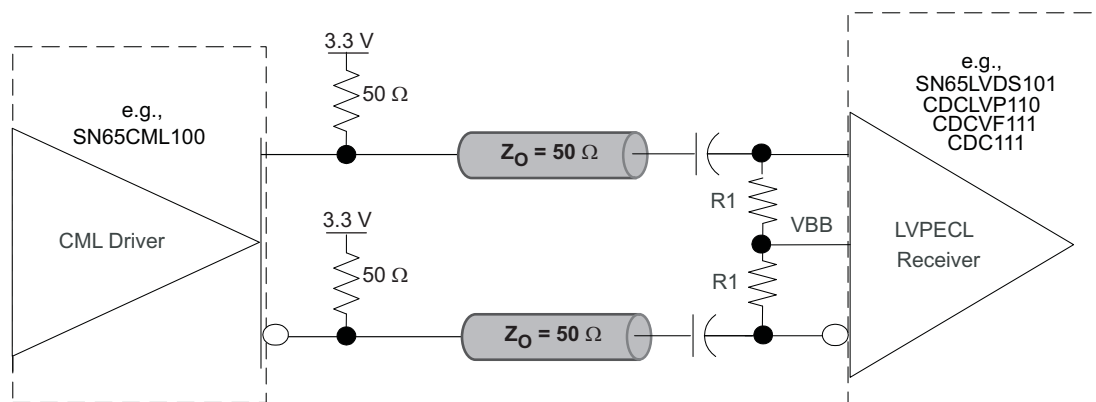


Figure 17. CML to LVPECL

The 50-Ω pull-up resistors are used to dc-bias and source-terminate the SN65CML100 outputs. The LVDS receiver has a wide input common-mode range (between 0 V and 2.4 V), that is, the receiver can accept any signal within the common-mode range and a differential swing of at least 100 mV. Figure 18, assumes a self-biased LVDS receiver.

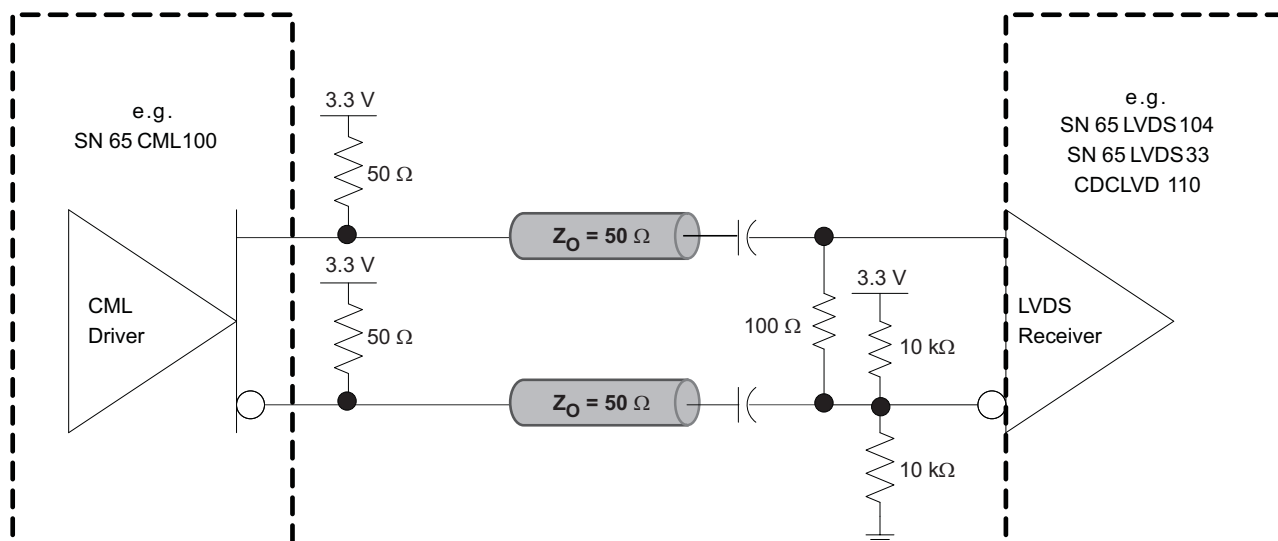


Figure 18. CML to LVDS

The 50- Ω pull-up resistors are required for the SN65CML100 to bias and source-terminate the transmission line. R1 in Figure 19 should be larger than 50 Ω in case the CML output stage losses, in addition to the PCB losses, are too high to meet the minimum (voltage input differential (VID) swing requirement of the LVDS input stage. Figure 19 assumes an internally generated bias voltage pin (VBB) is available.

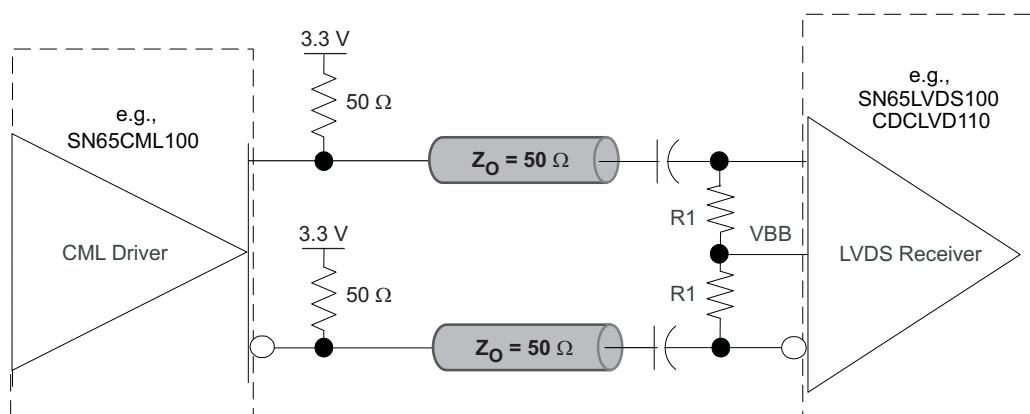


Figure 19. CML to LVDS

CML comes in many distinctions; therefore, termination and bias structures are not applicable to all CML drivers and receivers. The 50- Ω pull-up resistors, in Figure 20, are required to dc-bias the SN65CML100 and source-terminate the transmission line, while other CML drivers have integrated 50- Ω pull-up resistors, which do not require the external 50- Ω pull-up resistors.

The two 10-k Ω resistors are only required if the CML receiver is not self-biased and may vary from one vendor to another; see the manufacturer's data sheet for details.


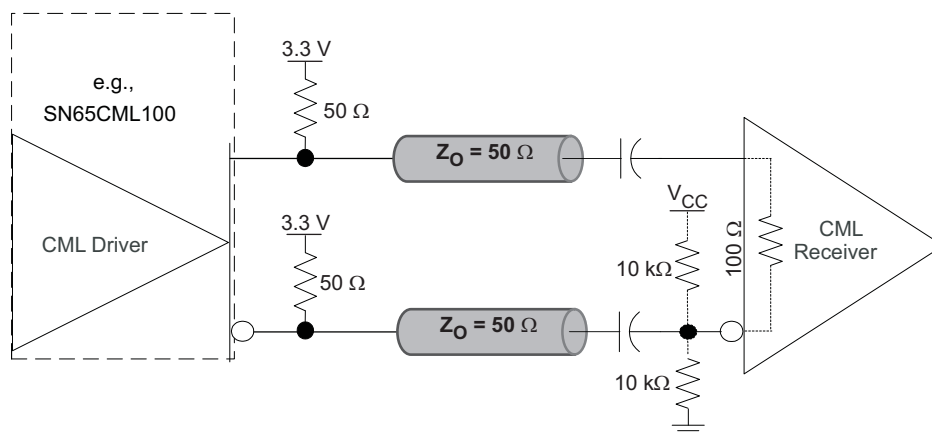


Figure 20. CML to CML

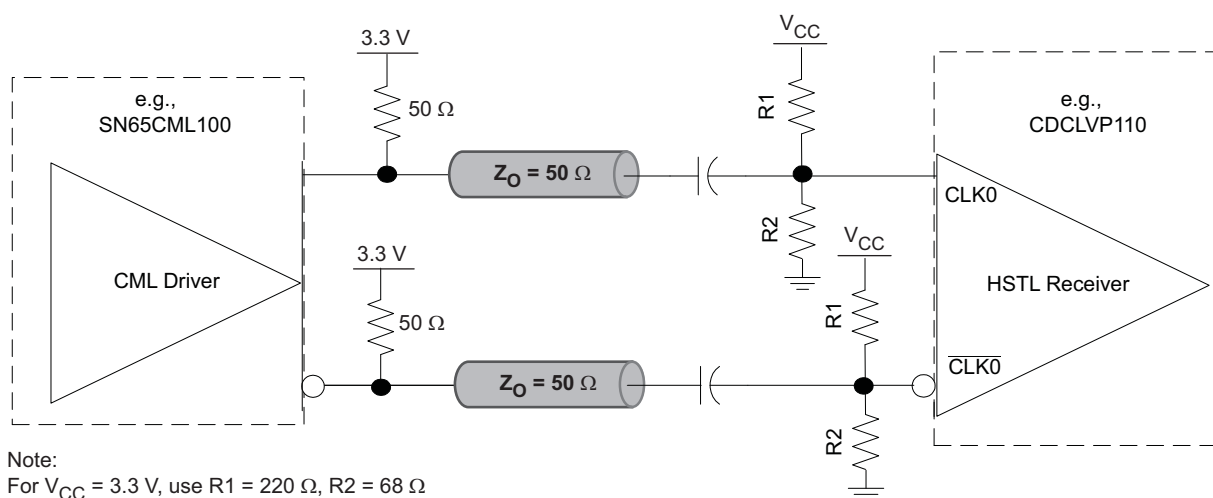In [Figure 21](#), the 50- Ω pull-up resistors are required to dc-bias the SN65CML100 outputs. The parallel combination of R1 and R2 are used to set the HSTL common-mode voltage ($V_{CM} = 0.75$ V).



Note:

For $V_{CC} = 3.3$ V, use $R1 = 220$ Ω , $R2 = 68$ Ω

For $V_{CC} = 2.5$ V, use $R1 = 167$ Ω , $R2 = 71$ Ω

For $V_{CC} = 1.5$ V, use $R1 = R2 = 100$ Ω

Figure 21. CML to HSTL

The 50- Ω pull-up resistors are required to dc-bias the SN65CML100 outputs. The split termination with the capacitor is useful in eliminating common-mode noise manifested as differential skew between the true and complementary signals. VBB output may be provided by HSTL receiver. R1 in [Figure 22](#) should be larger than 50 Ω when the CML output stage and the PCB losses are too high to meet the minimum voltage input differential (VID) swing requirement of the HSTL input stage.

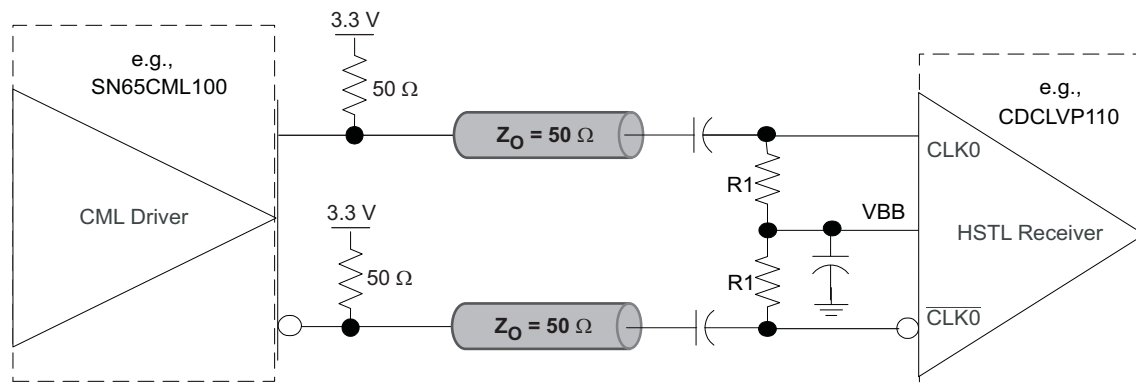


Figure 22. CML to HSTL

1.4 HSTL

In Figure 23, the split 50- Ω resistors are used to terminate the trace impedance as well as set the common-mode voltage ($V_{CM} = 2$) for the LVPECL receiver. The split termination with the capacitor is useful in eliminating common-mode noise manifested as differential skew between the true and complementary signals. VBB output is provided on most LVPECL receivers.

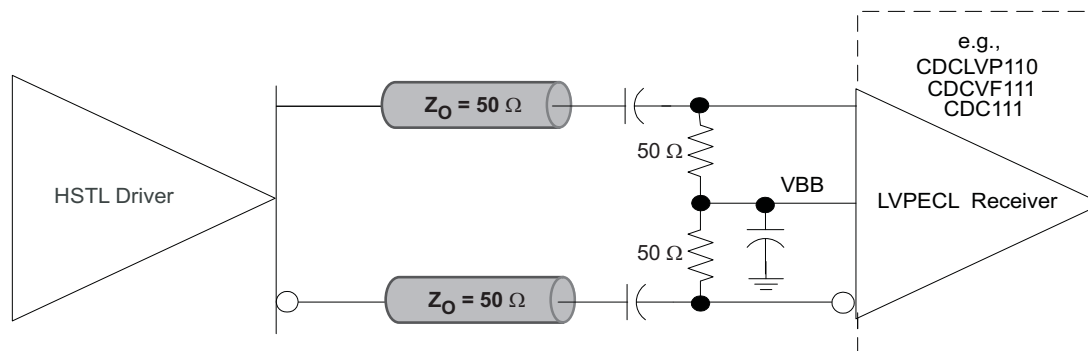


Figure 23. HSTL to LVPECL

The CDCLVP110 has a dual input that can accept either HSTL (CLK1 pair) or LVPECL input (CLK0 pair) levels and provide LVPECL output signals. The ac-coupling capacitors are not required for the CDCLVP110; nevertheless, they are included for completeness. The device functions properly without the coupling capacitors since the input stage of the CLK1 pair is optimized for HSTL input levels.

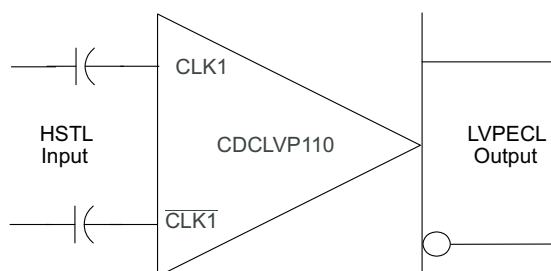


Figure 24. HSTL to LVPECL Converter

HSTL signals are usually terminated to ($V_{TT} = V_{ref} = 0.75\text{ V}$). Since most LVDS compatible receivers accept a 200-mV signal swing anywhere between 0 V and 2.4 V, then the HSTL signal is well within the LVDS receiver input range. The typical HSTL signal swing is 400 mV (minimum), 1.1 V (maximum) this amplitude is easily accepted by the LVDS receiver. The SN65LVDS100 requires a 3.3-V supply, while the CDCLVD110 is 2.5-V LVDS driver/receiver.

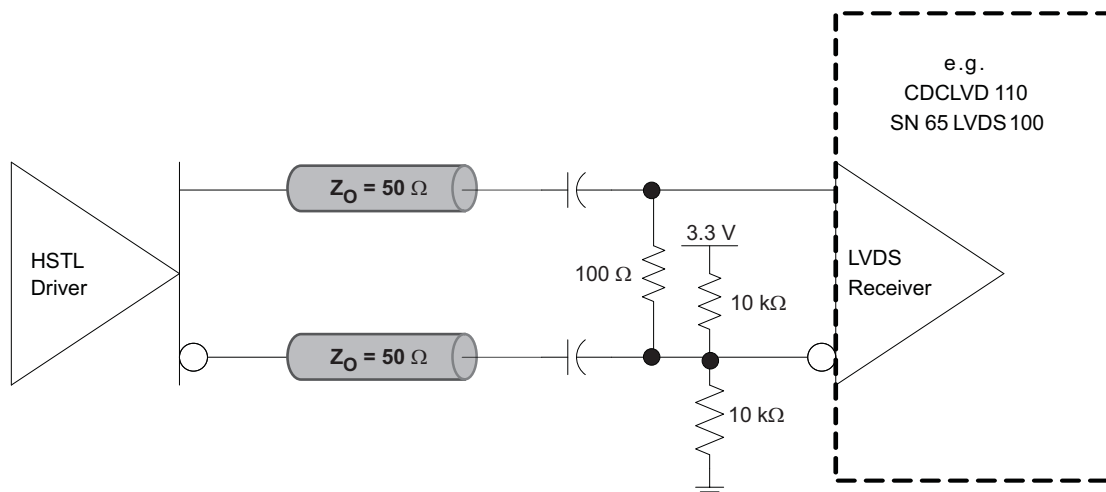


Figure 25. HSTL to LVDS

The split termination with capacitor in Figure 26 is recommended over Figure 25 in eliminating common-mode noise manifested as differential skew between the true and complementary signals. VBB output is provided on both the CDCLVD110 and the SN65LVDS100.

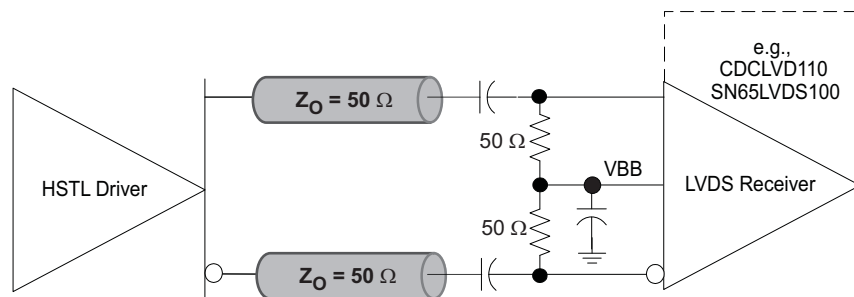


Figure 26. HSTL to LVDS

Both the SN65LVDS100 (3.3-V supply) and the CDCLVD110 (2.5-V supply) have wide input common-mode ranges and are capable of translating from HSTL to LVDS signaling levels.

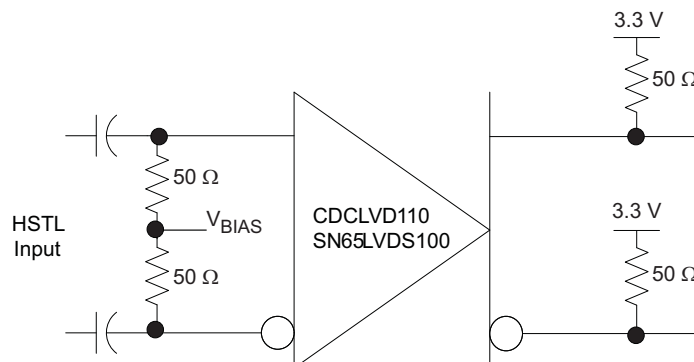


Figure 27. HSTL to LVDS Converter

The wide common-mode inputs range (0 V to 2.4 V) of the SN65CML100 can accept HSTL levels. If the 100- Ω resistor is not included on-chip, then it should be added externally in order to match the transmission line impedance for proper termination. The two 10-k Ω resistors are only required if the CML receiver is not self-biased and may vary from one vendor to another, see the manufacturer's data sheet for details.

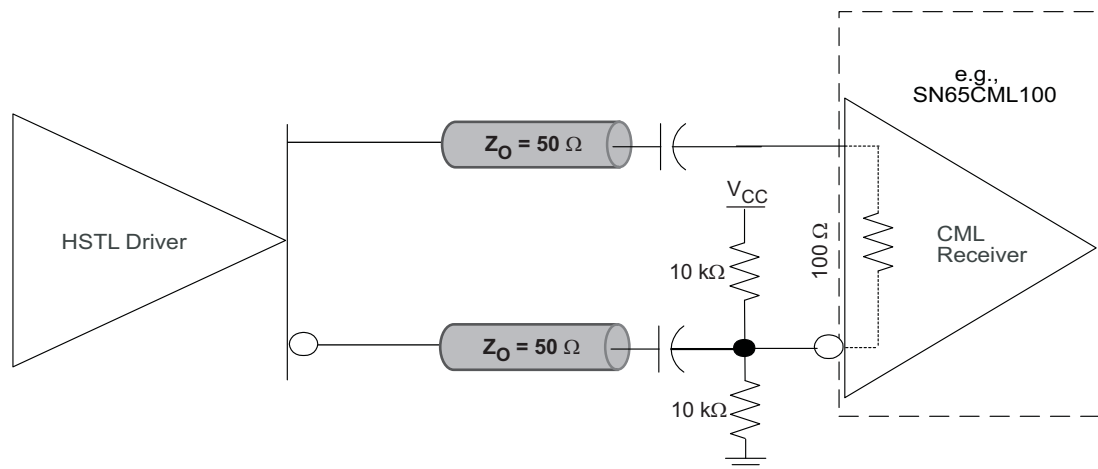


Figure 28. HSTL to CML

HSTL signals are terminated to VTT (typically 0.75 V). An alternative is 100 Ω across the differential pair or a split 50 Ω on each leg.

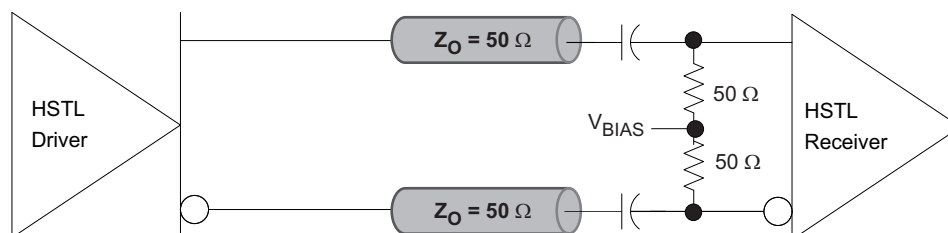


Figure 29. HSTL to HSTL

HSTL signals are usually terminated to (VTT = Vref = 0.75 V). The CDCLVP110 has a dual input that can accept either HSTL or LVPECL input levels and provide LVPECL output signals. The 150- Ω resistor is used to bias the LVPECL output (at VCC-1.3 V) as well as provide a dc current path for the source. The equivalent 50- Ω Thevenin resistors of R1 and R2 are used to terminate the trace impedance (the LVPECL output) and to set the common-mode voltage (VCM = 0.75 V) for the HSTL receiver.

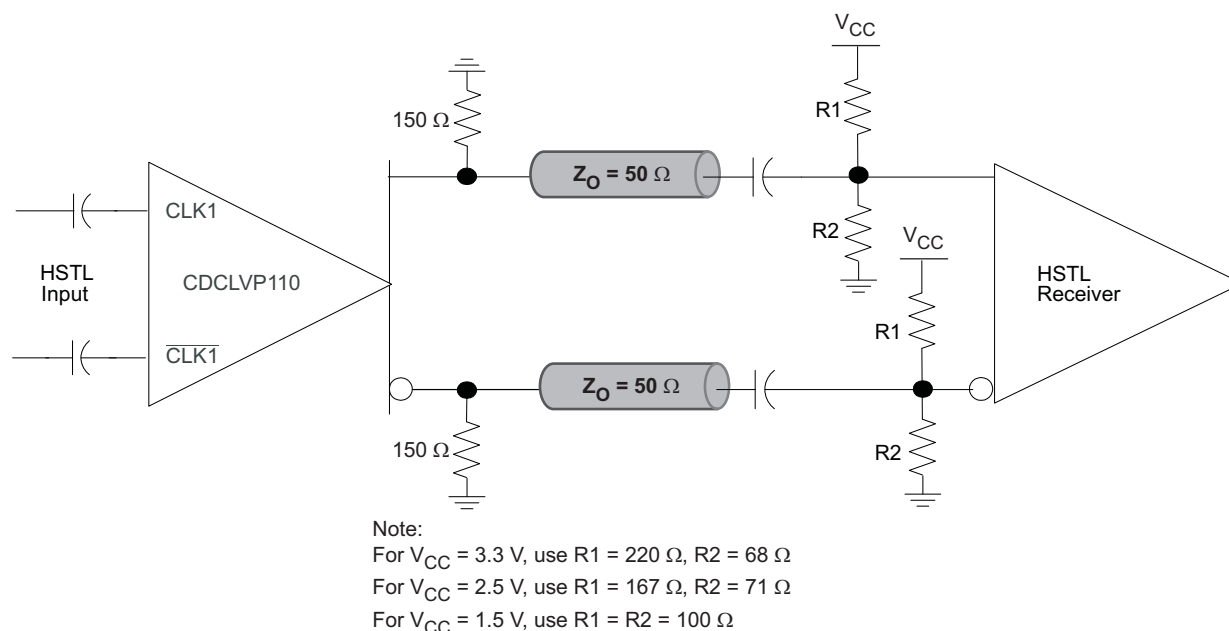


Figure 30. HSTL to LVPECL to HSTL Using the CDCLVP110

If the HSTL receiver has a 1.5-V supply, then R1 and R2 are 100 Ω each (equivalent 50 Ω) to match the trace impedance. For other supply voltages, R1 and R2 should be chosen such that their parallel combination matches the transmission line and the midpoint is set to the common mode of the HSTL receiver ($V_{CM} = 0.75\text{ V}$).

2 References

1. *Interfacing Between LVPECL, LVDS, and CML* application report, Texas Instruments ([SCAA056](#))
2. *Interfacing Differential Logic With LVDS Receivers*, Texas Instruments application report ([SLLA101](#))
3. *Clock Distribution Circuits (CDC)*, Texas Instruments CDC Data Book, ([SCAD004](#))
4. *DC-Coupling Between Differential LVPECL, LVDS, HSTL, and CML*, Texas Instruments application report ([SCAA062](#))
5. CDCLVD110 data sheet, Texas Instruments ([SCAS684](#))
6. CDCLVP110 data sheet, Texas Instruments ([SCAS683](#))
7. SN65LVDS100 data sheet, Texas Instruments ([SLLS516](#))
8. SN65CML100 data sheet, Texas Instruments ([SLLS547](#))
9. CDC111 data sheet, Texas Instruments ([SCAS321](#))
10. CDCVF111 data sheet, Texas Instruments ([SCAS670](#))
11. *Interfacing Between LVPECL, VML, CML, and LVDS Levels*; Texas Instruments application report ([SLLA120](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
Low Power Wireless	www.ti.com/lpw

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2007, Texas Instruments Incorporated