
Interfacing LVDS, LVPECL, CML, HCSL/LPHCSL

1.0 INTRODUCTION

When dealing with high-speed signaling, interconnects between components must be treated as transmission lines. Additionally, line termination must be considered with special care to avoid impedance mismatching and line discontinuities, which can lead to signal reflections and performance degradation.

This application note gives an overview of different transmission line termination techniques to interface between devices with similar or different I/O technologies (LVPECL, LVDS, CML, HCSL, LP-HCSL).

Proper line termination should maintain impedance matching and provide the right signal translation to avoid I/O incompatibilities which can lead to device malfunction, eventual reliability issues, and—in the worst case scenario—devices damage.

TABLE OF CONTENTS

Section 1.0, Introduction	1
Section 2.0, DC Coupling vs. AC Coupling	3
Section 3.0, Driver Output/Receiver Input Voltage Level	3
Section 4.0, DC Coupling	4
Section 4.1, DC Coupling LVDS Driver	4
Section 4.2, DC Coupling LVPECL Driver	7
Section 4.3, DC Coupling CML Driver	12
Section 4.4, DC Coupling HCSL/LPHCSL Driver	13
Section 5.0, AC Coupling	14
Section 5.1, AC Coupling LVDS Driver	14
Section 5.2, AC Coupling LVPECL Driver	16
Section 5.3, AC Coupling CML Driver	18
Section 5.4, AC Coupling HCSL Driver	21

2.0 DC COUPLING VS. AC COUPLING

DC coupling offers the advantage over AC coupling of less components count and less power consumption. However, while DC coupling, devices from different vendors or devices of different technology I/Os compatibility between driver's output signal level and receiver's input signal level range is not always guaranteed and, in some cases, comes with the price of adding more components with increase in power consumption and in many cases DC coupling is not possible at all leaving AC coupling as the only solution.

AC coupling blocks the DC bias between the driver's output and the receiver's input thus eliminating the issue of common mode voltage incompatibility between them. The receiver's input can then be biased at the optimum levels that offers the best performance in terms of jitter, duty cycle distortion, and crossing. While there is no issue with AC coupling clock signals, AC coupling data signals requires that the data be DC-balanced (same overall number of zeros and ones) to avoid signal decay, in the absence of transitions (during long chains of identical bits), at the two ends of the receiver termination to the same level, which will reduce noise margin.

3.0 DRIVER OUTPUT/RECEIVER INPUT VOLTAGE LEVEL

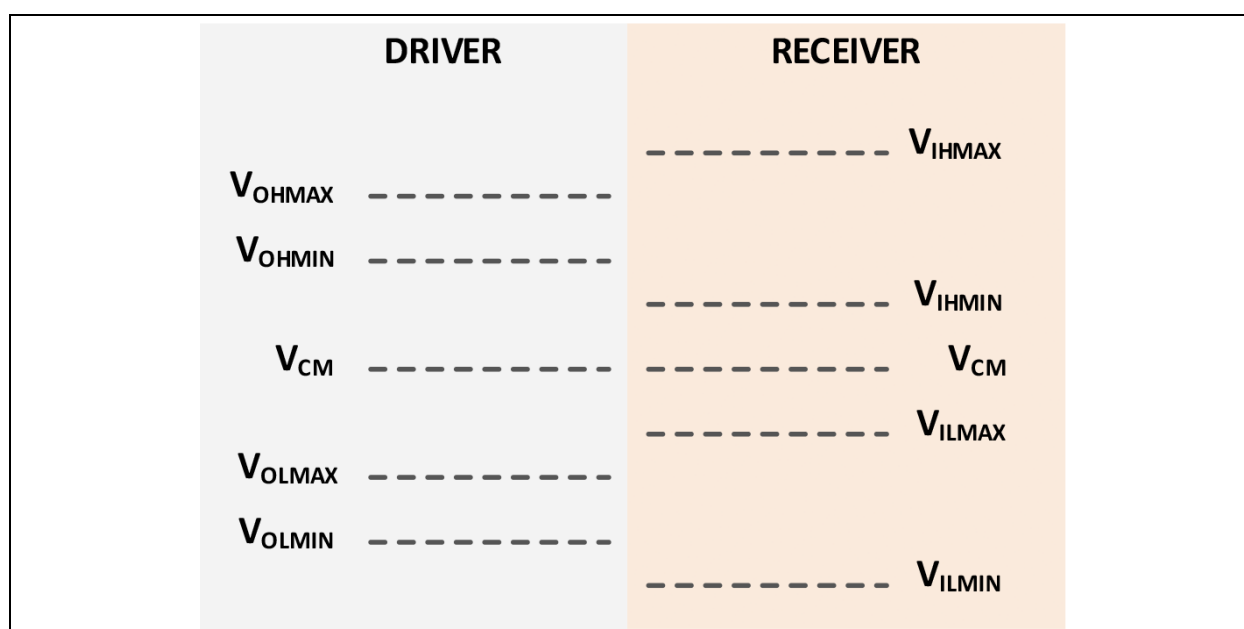


FIGURE 1: DRIVER'S OUTPUT AND RECEIVER'S INPUT VOLTAGE LEVEL.

Figure 1 shows the case where the driver's output and the receiver's input have the same common mode voltage and the driver's output signal levels fall within the receiver's input signal level range. This is the case we face when interfacing devices with the same logic especially when they are from the same manufacturer. It is the ideal case for DC coupling between the two devices.

Unfortunately, that's not always the case and sometimes even interfacing between devices of the same logic from different manufacturers requires special care when DC coupling. When the gap between the common mode voltage of the receiver's input and the common mode of the driver's output is too large, DC coupling becomes impossible, and AC coupling must be used to keep the driver and receiver at their sweet spots of operation. Figure 2 shows operating levels of most Microchip SYxxx products family that we'll be referring to in this application note.

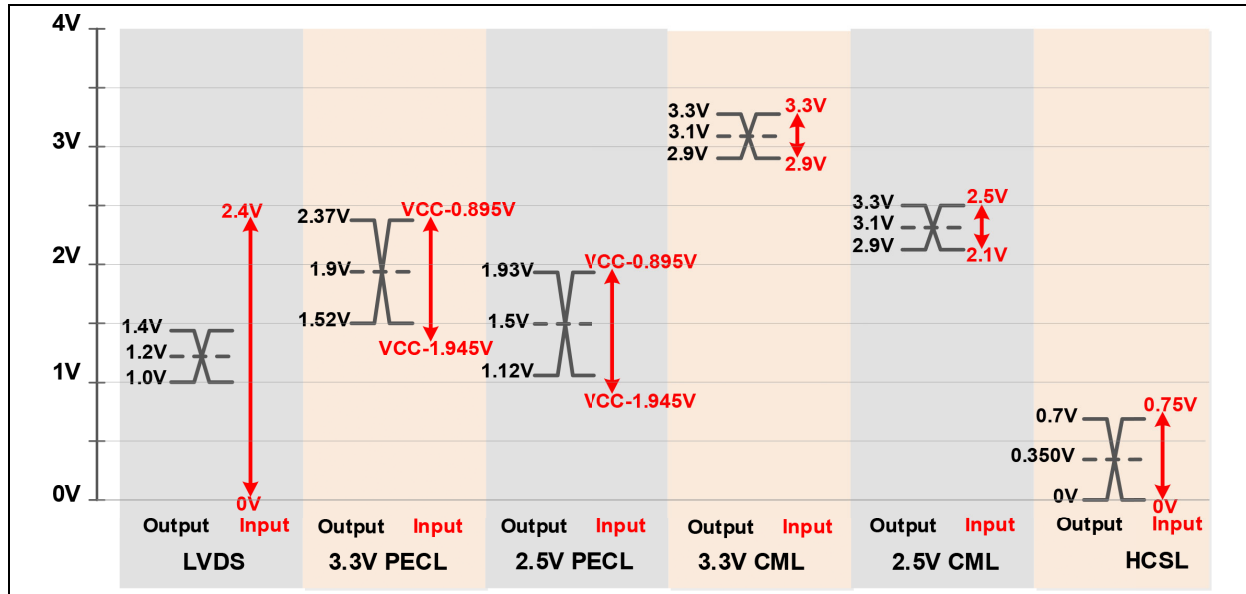


FIGURE 2: DIFFERENT I/O TECHNOLOGY INPUT/OUTPUT LEVELS.

4.0 DC COUPLING

4.1 DC Coupling LVDS Driver

4.1.1 DC COUPLING LVDS DRIVER TO LVDS RECEIVER

Just connect the LVDS output to the LVDS input and if the receiver doesn't have internal termination terminate with external 100Ω differential close to the receiver input.

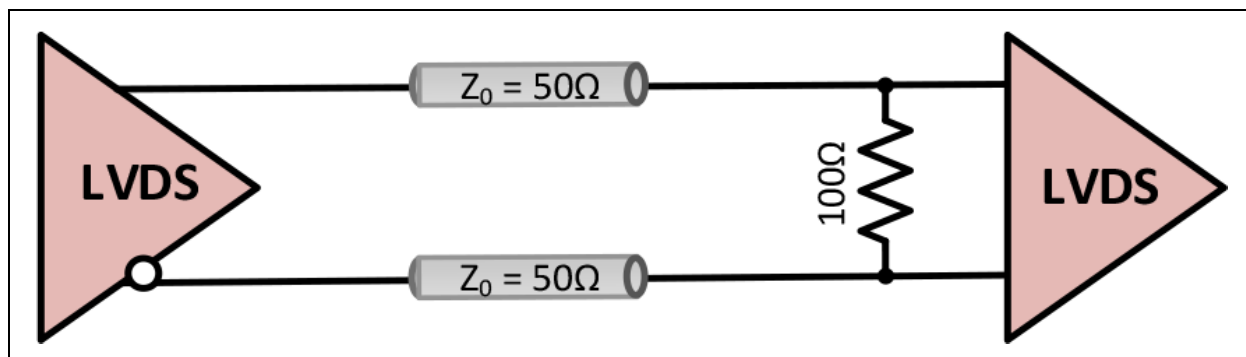


FIGURE 3: RECEIVER WITHOUT INTERNAL TERMINATION.

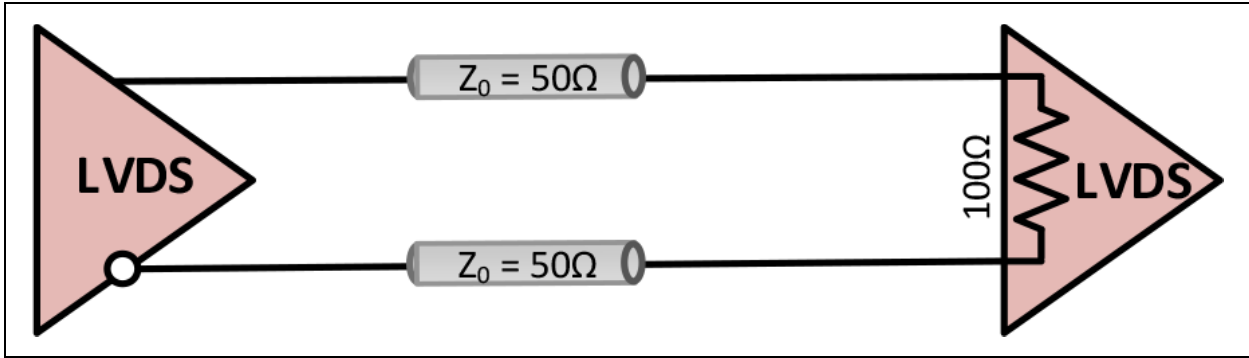


FIGURE 4: RECEIVER WITH INTERNAL TERMINATION.

4.1.2 DC COUPLING LVDS DRIVER TO LVPECL RECEIVER

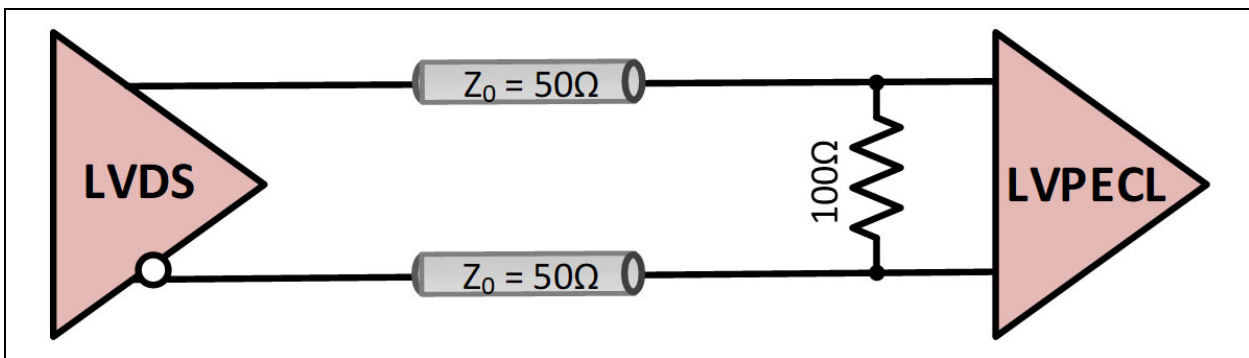


FIGURE 5: DC COUPLING LVDS TO LVPECL.

Even though the difference between the common mode voltage, 1.2V for LVDS vs $V_{CC}-1.3V$ for LVPECL, this circuit will work fine in most cases due to the wide common mode range of the LVPECL input and the relatively small swing of LVDS (400 mV) which will not cause the saturation of the LVPECL input stage current source.

Another solution to DC couple LVDS to LVPECL is to use a resistor network to shift the DC level from LVD common mode voltage (1.2V) to LVPECL common mode voltage ($V_{CC}-1.3V$). This can be achieved using the circuit in Figure 6. Resistors values can be calculated from the following equations dictated by the circuit constraints:

LVDS common mode voltage at point A:

EQUATION 1:

$$\frac{R1}{R2 + R3} \times V_{CC} = 1.2V$$

LVPECL common mode voltage at point B:

EQUATION 2:

$$\frac{R1 + R2}{R1 + R2 + R3} \times V_{CC} = V_{CC} - 1.3V$$

EQUATION 3:

$$\left(\frac{R_0}{2}\right) \parallel (R_1 \parallel (R_2 + R_3)) = 50$$

Considering $V_{CC} = 3.3V$ and solving Equation 1 and Equation 2 leads to $R_2 = 0.615R_3$ and $R_1 = 0.571 (R_2 + R_3)$. For $R_2 = 200\Omega$, $R_3 = 325\Omega$ (324 Ω normalized), and $R_1 = 299\Omega$ (301 Ω normalized). Then, Equation 3 leads to $R_0 = 136\Omega$ (137 Ω normalized).

Selecting high value resistors has the advantage of low power consumption while lower value resistors allow the circuit to perform better at higher frequencies.

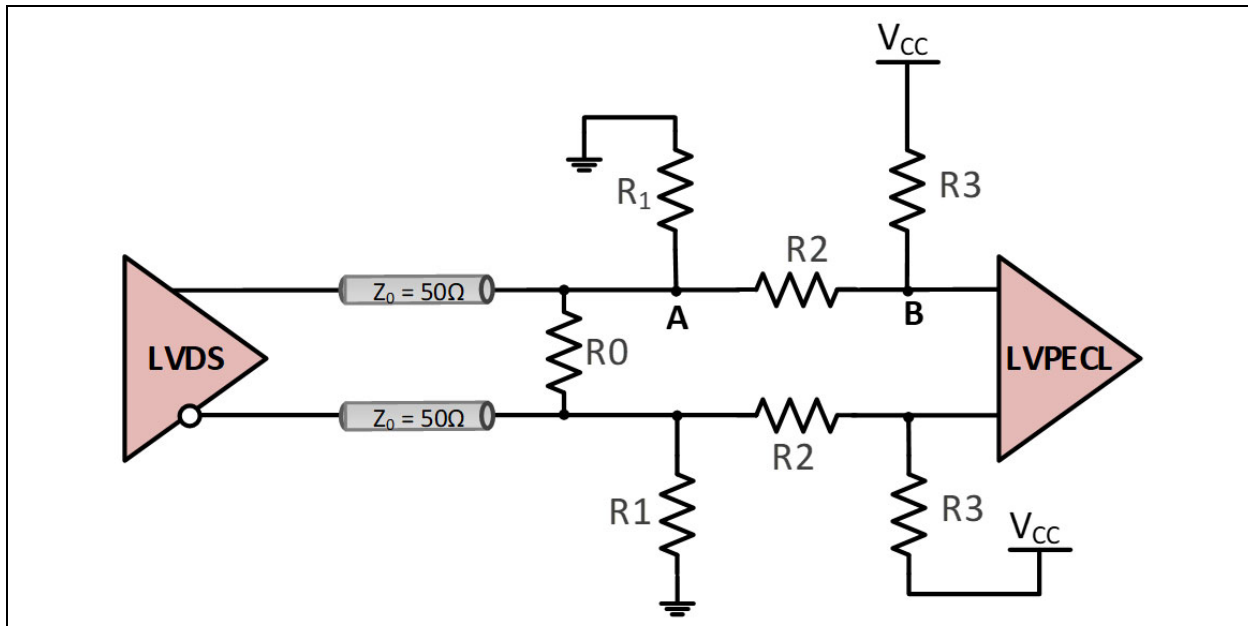


FIGURE 6: DC COUPLING LVDS DRIVER TO CML RECEIVER.

4.1.3 DC COUPLING LVDS DRIVER TO CML RECEIVER

Due to the large gap between the LVDS and CML common mode voltage it's not practical to DC couple LVDS driver to CML receiver and vice versa.

4.2 DC Coupling LVPECL Driver

4.2.1 DC COUPLING LVPECL DRIVER TO LVPECL RECEIVER

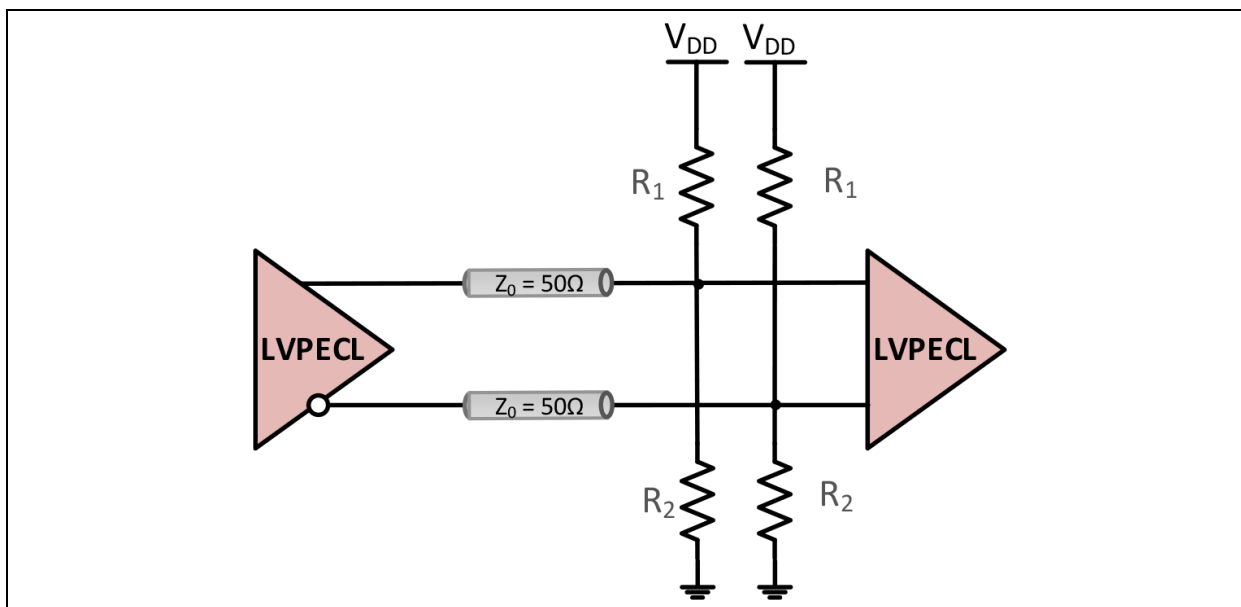


FIGURE 7: DC COUPLING LVPECL TO LVPECL.

 


FIGURE 8: DC COUPLING LVPECL TO LVPECL.

In [Figure 7](#), the Thevenin termination is equivalent to the 50Ω to $V_{CC} - 2V$ standard LVPECL termination and satisfy [Equation 4](#) and [Equation 5](#).

EQUATION 4:

$$\frac{R_1 \times R_2}{R_1 + R_2} = 50$$

EQUATION 5:

$$\frac{R2}{R1 + R2} \times V_{CC} = V_{CC} - 2$$

The R1 and R2 solutions are:

$$R1 = \frac{50 \times V_{CC}}{V_{CC} - 2}$$

$$R2 = 25 \times V_{CC}$$

For $V_{CC} = 3.3V$: $R1 = 127\Omega$, $R2 = 82.5\Omega$

In [Figure 8](#), the value of R is calculated as follows:

The voltage at the node between R and the 50Ω is $V_{CC} - 2V$ (PECL termination: 50Ω to $V_{CC} - 2V$) and the current flowing through R is the sum of the currents flowing through the two 50Ω termination resistors.

EQUATION 6:

$$I = \frac{V_{OH} - (V_{CC} - 2)}{50} + \frac{V_{OL} - (V_{CC} - 2)}{50}$$

$$I = \frac{(V_{OH} + V_{OL}) - (2V_{CC} + 4)}{50}$$

EQUATION 7:

$$R = \frac{V_{CC} - 2}{1} = \frac{50 \times (V_{CC} - 2)}{(V_{OH} + V_{OL}) - (2V_{CC} + 4)}$$

If we consider SY58012U as a driver, the following table shows R0 values for $V_{CC} = 3.3V$ and $2.5V$.

TABLE 4-1: RO VALUES FOR $V_{CC} = 3.3V$ AND $2.5V$

V_{CC}	V_{OH}	V_{OL}	R
3.3V	$V_{CC} - 0.895V$	$V_{CC} - 1.695V$	40 Ω
2.5V			18 Ω

4.2.2 DC COUPLING LVPECL DRIVER TO LVDS RECEIVER

 


FIGURE 9: DC COUPLING LVPECL TO LVDS.

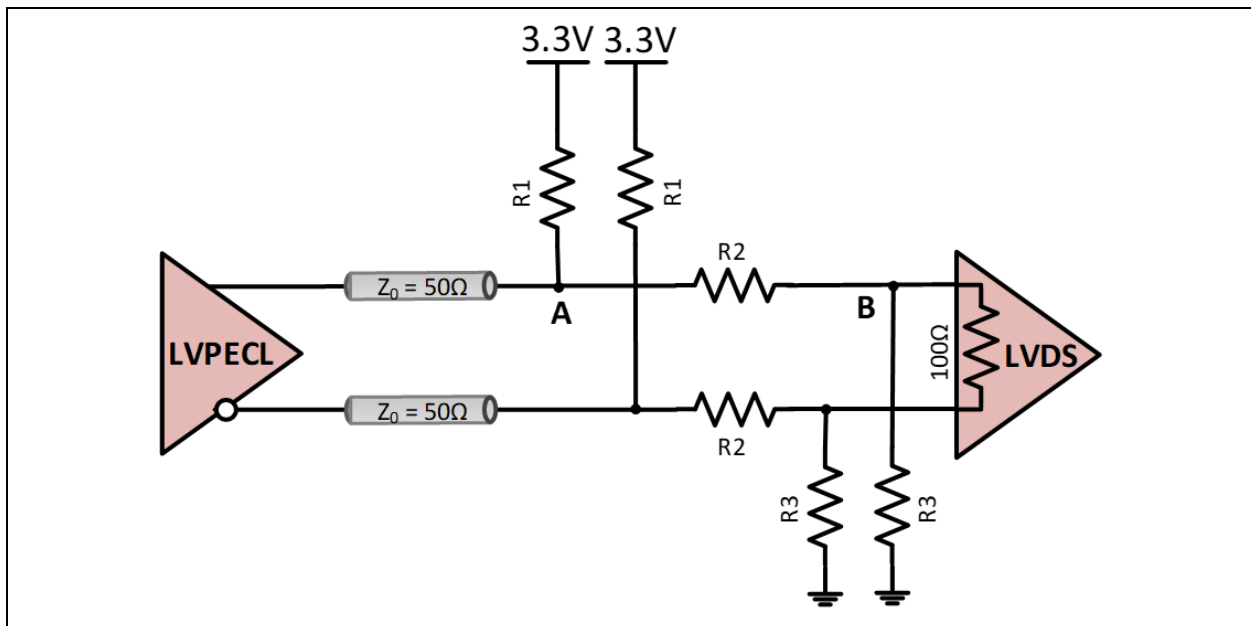


FIGURE 10: DC COUPLING LVPECL TO LVDS WITH INTERNAL DIFFERENTIAL 100Ω TERMINATION.

The voltages at nodes A and B in both [Figure 9](#) and [Figure 10](#) are:

- A: $V_{CM}(\text{LVPECL}) = V_{CC} - 1.3V = 2V$
- B: $V_{CM}(\text{LVDS}) = 1.2V$

AN5020

In [Figure 9](#), we have the following:

EQUATION 8:

$$(R2 + R3)/(R1 + R2 + R3) \times 3.3 = 2$$

EQUATION 9:

$$R3 \parallel (R1 + R2 + R3) \times 2 = 1.2$$

EQUATION 10:

$$R1 \parallel (R2 + R3) = 50$$

The values of R1, R2, and R3 satisfying [Equation 8](#), [Equation 9](#), and [Equation 10](#) for [Figure 9](#) are:

- R1 = 82.5Ω
- R2 = 51Ω
- R3 = 75.8Ω

In [Figure 10](#), where the receiver has internal differential 100Ω termination, we have:

EQUATION 11:

$$(R2 + R3)/(R1 + R2 + R3) \times 3.3 = 2$$

EQUATION 12:

$$(R3)/(R1 + R2 + R3) \times 2 = 1.2$$

EQUATION 13:

$$R1 \parallel (R2 + R3 \parallel 50) = 50$$

The values of R1, R2, and R3 satisfying Equation 11, Equation 12, and Equation 13 for Figure 10 are:

- R1 = 102Ω
- R2 = 63.4Ω
- R3 = 95.3Ω

4.2.3 DC COUPLING LVPECL DRIVER TO CML RECEIVER

It is not recommended to DC couple LVPECL to CML unless AC coupling cannot be used due, for example, to unbalanced data. In this case, the diagram in Figure 11 can be used. From the LVPECL output, the resistor network is seen as a Thevenin termination with 82.5Ω to GND and 208 // (275 + 50) = 127Ω to VCC. The CML input is biased with the 50Ω to VCC.

 


FIGURE 11: DC COUPLING LVPECL TO CML.

4.3 DC Coupling CML Driver

4.3.1 DC COUPLING CML DRIVER TO CML RECEIVER

 


FIGURE 12: DC COUPLING CML TO CML (DRIVER WITH INTERNAL TERMINATION).

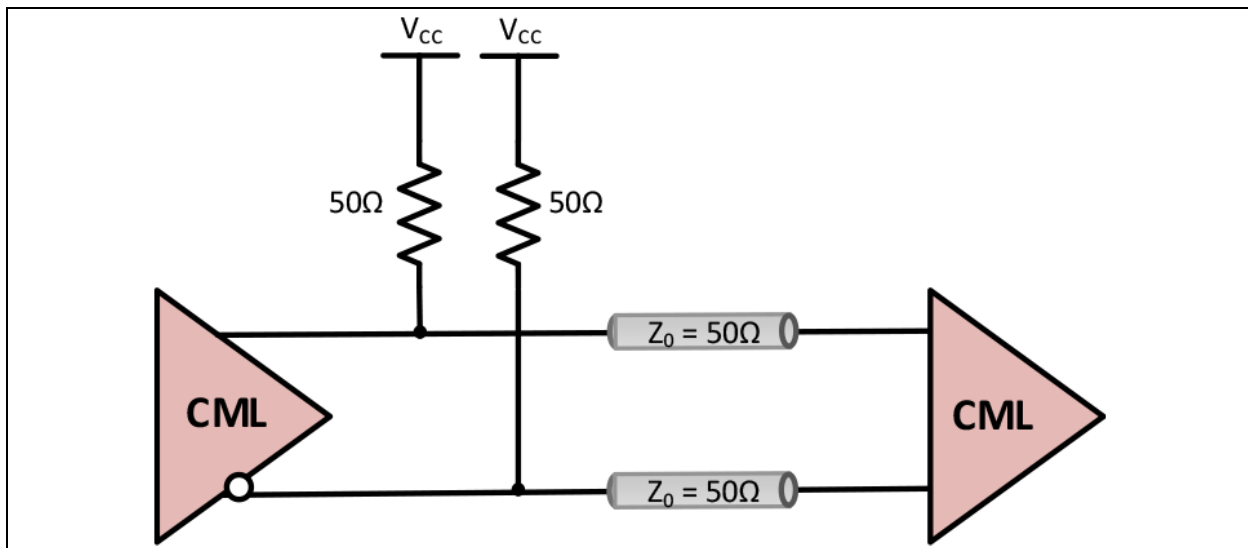


FIGURE 13: DC COUPLING CML TO CML (DRIVER WITHOUT INTERNAL TERMINATION).

Due to the high common mode voltage of the CML driver ($V_{CC} - 200\text{ mV}$), it's difficult if not impossible to DC couple the CML driver to other logics.

4.4 DC Coupling HCSL/LPHCSL Driver

4.4.1 DC COUPLING HCSL/LPHCSL DRIVER TO HCSL RECEIVER

 


FIGURE 14: DC COUPLING HCSL TO HCSL.

 


FIGURE 15: DC COUPLING LPHCSL TO HCSL.

LPHCSL doesn't require the 50Ω termination to GND necessary for the HCSL driver, which needs a path to ground.

Due to the low common mode voltage of the HCSL/LPHCSL driver (250 mV – 55 mV), it's difficult if not impossible to DC couple the HCSL/LPHCSL driver to other logics.

5.0 AC COUPLING

5.1 AC Coupling LVDS Driver

5.1.1 AC COUPLING LVDS DRIVER TO LVDS RECEIVER

 


FIGURE 16: AC COUPLING LVDS TO LVDS.

For an LVDS receiver without internal termination, the termination network in [Figure 16](#) sets the appropriate termination at the receiver input and sets the LVDS input common mode voltage (1.2V). If the receiver has internal termination, the external network used to generate the common mode voltage (1.2V) should use high value resistors to preserve the transmission line termination (100Ω differential). In [Figure 17](#), the 5.1KΩ and 9.1KΩ resistor values set the common mode voltage to 1.2V.

 
 



FIGURE 17: AC COUPLING LVDS TO LVDS (RECEIVER WITH INTERNAL TERMINATION).

5.1.2 AC COUPLING LVDS DRIVER TO LVPECL RECEIVER

**FIGURE 18: AC COUPLING LVDS TO LVPECL.**

The termination network in [Figure 18](#) restores the LVPECL input common mode voltage ($V_{CC} - 1.3V = 2V$) and provide 50Ω line termination (100Ω differential). If the receiver has a V_{BB} (2V) bias source, just terminate each input with a 50Ω to V_{BB} . To interface to Microchip SYxxx products with “Any IN Input” with internal 50Ω termination to V_T and V_{REF_AC} pin, just connect the V_T pin to the V_{REF_AC} pin.

5.1.3 AC COUPLING LVDS DRIVER TO CML RECEIVER

 **FIGURE 19: AC COUPLING LVDS TO CML.**

The 50Ω resistors provide the bias to the CML input and the 100Ω differential termination to the LVDS driver.

5.1.4 AC COUPLING LVDS DRIVER TO HCSL RECEIVER

 


FIGURE 20: AC COUPLING LVDS TO HCSL.

The 471Ω/56Ω network sets the HCSL receiver common mode voltage to about 400 mV.

5.2 AC Coupling LVPECL Driver

5.2.1 AC COUPLING LVPECL DRIVER TO LVPECL RECEIVER

 


FIGURE 21: AC COUPLING LVPECL TO LVPECL.

The 82.5Ω/127Ω network terminates the line with 50Ω and sets the LVPECL input common mode voltage to $V_{CC} - 1.3V$ (2V).

5.2.2 AC COUPLING LVPECL DRIVER TO LVDS RECEIVER

 


FIGURE 22: AC COUPLING LVPECL TO LVDS.

The 150Ω is the equivalent termination to LVPECL output. The 5.1KΩ/9.1KΩ network sets the LVDS input common mode voltage to 1.2V.

5.2.3 AC COUPLING LVPECL DRIVER TO CML RECEIVER

 


FIGURE 23: AC COUPLING LVPECL TO CML.

The 50Ω resistors terminate the line and bias the CML input while the series resistor attenuates the LVPECL signal to be within range for CML input.

5.2.4 AC COUPLING LVPECL DRIVER TO HCSSL RECEIVER

 


FIGURE 24: AC COUPLING LVPECL TO HCSSL.

The 471Ω/56Ω network provide a 50Ω line termination and set the HCSSL input common voltage close to 400 mV.

5.3 AC Coupling CML Driver

5.3.1 AC COUPLING CML DRIVER TO CML RECEIVER

 


FIGURE 25: AC COUPLING CML TO CML (DRIVER WITH INTEGRATED 50Ω TERMINATION TO VCC).

 


FIGURE 26: AC COUPLING CML TO CML (DRIVER WITHOUT INTEGRATED 50Ω TERMINATION TO VCC).

If the driver doesn't have internal 50Ω termination to VCC, the output must be terminated outside before the coupling cap.

5.3.2 AC COUPLING CML DRIVER TO LVDS RECEIVER

 


FIGURE 27: AC COUPLING CML TO LVDS.

The CML driver in [Figure 27](#) has internal 50Ω termination to VCC, and the LVDS receiver doesn't have internal termination. The 5.1 KΩ/9.1 KΩ networks set the 1.2V common mode voltage for the LVDS receiver. For CML driver without internal termination, please refer to [Figure 26](#). For an LVDS receiver with internal termination, please refer to [Figure 17](#).

5.3.3 AC COUPLING CML DRIVER TO LVPECL RECEIVER

 


FIGURE 28: AC COUPLING CML TO LVPECL.

5.3.4 AC COUPLING CML DRIVER TO HCSL RECEIVER

 


FIGURE 29: AC COUPLING CML TO HCSL.

5.4 AC Coupling HCSL Driver

5.4.1 AC COUPLING HCSL DRIVER TO HCSL RECEIVER

 


FIGURE 30: AC COUPLING HCSL TO HCSL.

5.4.2 AC COUPLING HCSL DRIVER TO LVDS RECEIVER

 


FIGURE 31: AC COUPLING HCSL TO LVDS.

 


FIGURE 32: AC COUPLING LPHCSL TO LVDS.

5.4.3 AC COUPLING HCSL DRIVER TO LVPECL RECEIVER

 


FIGURE 33: AC COUPLING HCSL TO LVPECL.

5.4.4 AC COUPLING HCSL DRIVER TO CML RECEIVER

 


FIGURE 34: AC COUPLING HCSL TO CML.

AN5020

NOTES:

Note the following details of the code protection feature on Microchip products:

- Microchip products meet the specifications contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is secure when used in the intended manner, within operating specifications, and under normal conditions.
- Microchip values and aggressively protects its intellectual property rights. Attempts to breach the code protection features of Microchip product is strictly prohibited and may violate the Digital Millennium Copyright Act.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of its code. Code protection does not mean that we are guaranteeing the product is “unbreakable”. Code protection is constantly evolving. Microchip is committed to continuously improving the code protection features of our products.

This publication and the information herein may be used only with Microchip products, including to design, test, and integrate Microchip products with your application. Use of this information in any other manner violates these terms. Information regarding device applications is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. Contact your local Microchip sales office for additional support or, obtain additional support at <https://www.microchip.com/en-us/support/design-help/client-support-services>.

THIS INFORMATION IS PROVIDED BY MICROCHIP “AS IS”. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION INCLUDING BUT NOT LIMITED TO ANY IMPLIED WARRANTIES OF NON-INFRINGEMENT, MERCHANTABILITY, AND FITNESS FOR A PARTICULAR PURPOSE, OR WARRANTIES RELATED TO ITS CONDITION, QUALITY, OR PERFORMANCE.

IN NO EVENT WILL MICROCHIP BE LIABLE FOR ANY INDIRECT, SPECIAL, PUNITIVE, INCIDENTAL, OR CONSEQUENTIAL LOSS, DAMAGE, COST, OR EXPENSE OF ANY KIND WHATSOEVER RELATED TO THE INFORMATION OR ITS USE, HOWEVER CAUSED, EVEN IF MICROCHIP HAS BEEN ADVISED OF THE POSSIBILITY OR THE DAMAGES ARE FORESEEABLE. TO THE FULLEST EXTENT ALLOWED BY LAW, MICROCHIP’S TOTAL LIABILITY ON ALL CLAIMS IN ANY WAY RELATED TO THE INFORMATION OR ITS USE WILL NOT EXCEED THE AMOUNT OF FEES, IF ANY, THAT YOU HAVE PAID DIRECTLY TO MICROCHIP FOR THE INFORMATION.

Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights unless otherwise stated.

Trademarks

The Microchip name and logo, the Microchip logo, Adaptec, AnyRate, AVR, AVR logo, AVR Freaks, BesTime, BitCloud, CryptoMemory, CryptoRF, dsPIC, flexPWR, HELDO, IGLOO, JukeBlox, KeeLoq, Klear, LANCheck, LinkMD, maxStylus, maxTouch, MediaLB, megaAVR, Microsemi, Microsemi logo, MOST, MOST logo, MPLAB, OptoLyzer, PIC, picoPower, PICSTART, PIC32 logo, PolarFire, Prochip Designer, QTouch, SAM-BA, SenGenuity, SpyNIC, SST, SST Logo, SuperFlash, Symmetricom, SyncServer, Tachyon, TimeSource, tinyAVR, UNI/O, Vectron, and XMEGA are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

AgileSwitch, APT, ClockWorks, The Embedded Control Solutions Company, EtherSynch, Flashtec, Hyper Speed Control, HyperLight Load, IntelliMOS, Libero, motorBench, mTouch, Powermite 3, Precision Edge, ProASIC, ProASIC Plus, ProASIC Plus logo, Quiet-Wire, SmartFusion, SyncWorld, Temux, TimeCesium, TimeHub, TimePictra, TimeProvider, TrueTime, WinPath, and ZL are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Adjacent Key Suppression, AKS, Analog-for-the-Digital Age, Any Capacitor, AnyIn, AnyOut, Augmented Switching, BlueSky, BodyCom, CodeGuard, CryptoAuthentication, CryptoAutomotive, CryptoCompanion, CryptoController, dsPICDEM, dsPICDEM.net, Dynamic Average Matching, DAM, ECAN, Espresso T1S, EtherGREEN, GridTime, IdealBridge, In-Circuit Serial Programming, ICSP, INICnet, Intelligent Paralleling, Inter-Chip Connectivity, JitterBlocker, Knob-on-Display, maxCrypto, maxView, memBrain, Mindi, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, NVM Express, NVMe, Omniscient Code Generation, PICDEM, PICDEM.net, PICkit, PICtail, PowerSmart, PureSilicon, QMatrix, REAL ICE, Ripple Blocker, RTAX, RTG4, SAM-ICE, Serial Quad I/O, simpleMAP, SimpliPHY, SmartBuffer, SmartHLS, SMART-I.S., storClad, SQL, SuperSwitcher, SuperSwitcher II, Switchtec, SynchroPHY, Total Endurance, TSHARC, USBCheck, VariSense, VectorBlox, VeriPHY, ViewSpan, WiperLock, XpressConnect, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

The Adaptec logo, Frequency on Demand, Silicon Storage Technology, Symmcom, and Trusted Time are registered trademarks of Microchip Technology Inc. in other countries.

GestIC is a registered trademark of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2023, Microchip Technology Incorporated and its subsidiaries. All Rights Reserved.

ISBN: 978-1-6683-3462-1

For information regarding Microchip’s Quality Management Systems, please visit www.microchip.com/quality.

Worldwide Sales and Service

AMERICAS

Corporate Office
2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://www.microchip.com/support>
Web Address:
www.microchip.com

Atlanta
Duluth, GA
Tel: 678-957-9614
Fax: 678-957-1455

Austin, TX
Tel: 512-257-3370

Boston
Westborough, MA
Tel: 774-760-0087
Fax: 774-760-0088

Chicago
Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Dallas
Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit
Novi, MI
Tel: 248-848-4000

Houston, TX
Tel: 281-894-5983

Indianapolis
Noblesville, IN
Tel: 317-773-8323
Fax: 317-773-5453
Tel: 317-536-2380

Los Angeles
Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608
Tel: 951-273-7800

Raleigh, NC
Tel: 919-844-7510

New York, NY
Tel: 631-435-6000

San Jose, CA
Tel: 408-735-9110
Tel: 408-436-4270

Canada - Toronto
Tel: 905-695-1980
Fax: 905-695-2078

ASIA/PACIFIC

Australia - Sydney
Tel: 61-2-9868-6733

China - Beijing
Tel: 86-10-8569-7000

China - Chengdu
Tel: 86-28-8665-5511

China - Chongqing
Tel: 86-23-8980-9588

China - Dongguan
Tel: 86-769-8702-9880

China - Guangzhou
Tel: 86-20-8755-8029

China - Hangzhou
Tel: 86-571-8792-8115

China - Hong Kong SAR
Tel: 852-2943-5100

China - Nanjing
Tel: 86-25-8473-2460

China - Qingdao
Tel: 86-532-8502-7355

China - Shanghai
Tel: 86-21-3326-8000

China - Shenyang
Tel: 86-24-2334-2829

China - Shenzhen
Tel: 86-755-8864-2200

China - Suzhou
Tel: 86-186-6233-1526

China - Wuhan
Tel: 86-27-5980-5300

China - Xian
Tel: 86-29-8833-7252

China - Xiamen
Tel: 86-592-2388138

China - Zhuhai
Tel: 86-756-3210040

ASIA/PACIFIC

India - Bangalore
Tel: 91-80-3090-4444

India - New Delhi
Tel: 91-11-4160-8631

India - Pune
Tel: 91-20-4121-0141

Japan - Osaka
Tel: 81-6-6152-7160

Japan - Tokyo
Tel: 81-3-6880-3770

Korea - Daegu
Tel: 82-53-744-4301

Korea - Seoul
Tel: 82-2-554-7200

Malaysia - Kuala Lumpur
Tel: 60-3-7651-7906

Malaysia - Penang
Tel: 60-4-227-8870

Philippines - Manila
Tel: 63-2-634-9065

Singapore
Tel: 65-6334-8870

Taiwan - Hsin Chu
Tel: 886-3-577-8366

Taiwan - Kaohsiung
Tel: 886-7-213-7830

Taiwan - Taipei
Tel: 886-2-2508-8600

Thailand - Bangkok
Tel: 66-2-694-1351

Vietnam - Ho Chi Minh
Tel: 84-28-5448-2100

EUROPE

Austria - Wels
Tel: 43-7242-2244-39
Fax: 43-7242-2244-393

Denmark - Copenhagen
Tel: 45-4485-5910
Fax: 45-4485-2829

Finland - Espoo
Tel: 358-9-4520-820

France - Paris
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Garching
Tel: 49-8931-9700

Germany - Haan
Tel: 49-2129-3766400

Germany - Heilbronn
Tel: 49-7131-72400

Germany - Karlsruhe
Tel: 49-721-625370

Germany - Munich
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Germany - Rosenheim
Tel: 49-8031-354-560

Israel - Ra'anana
Tel: 972-9-744-7705

Italy - Milan
Tel: 39-0331-742611
Fax: 39-0331-466781

Italy - Padova
Tel: 39-049-7625286

Netherlands - Drunen
Tel: 31-416-690399
Fax: 31-416-690340

Norway - Trondheim
Tel: 47-7288-4388

Poland - Warsaw
Tel: 48-22-3325737

Romania - Bucharest
Tel: 40-21-407-87-50

Spain - Madrid
Tel: 34-91-708-08-90
Fax: 34-91-708-08-91

Sweden - Gothenberg
Tel: 46-31-704-60-40

Sweden - Stockholm
Tel: 46-8-5090-4654

UK - Wokingham
Tel: 44-118-921-5800
Fax: 44-118-921-5820